

## Experiment-2

AIM: To realize Half Adder and Full Adder

LEARNING OBJECTIVE: To realize the adder and subtractor circuits using basic gates and universal gates. To realize full adder using two half adders. To realize a full subtractor using two half subtractors.

**THEORY:** Half-Adder: A combinational logic circuit that performs the addition of two data bits, A and B, is called a half-adder. Addition will result in two output bits; one of which is the sum bit, S, and the other is the carry bit, C. The Boolean functions describing the half-adder are:  $S = A \oplus B$   $C = A \cdot B$  Full-Adder: The half-adder does not take the carry bit from its previous stage into account. This carry bit from its previous stage is called carry-in bit. A combinational logic circuit that adds two data bits, A and B, and a carry-in bit, Cin, is called a full-adder. The Boolean functions describing the full-adder are:  $S = (x \oplus y) \oplus Cin$   $C = xy + Cin(x \oplus y)$  Half Subtractor: Subtracting a single-bit binary value B from another A (i.e.  $A - B$ ) produces a difference bit D and a borrow out bit B-out. This operation is called half subtraction and the circuit to realize it is called a half subtractor. The Boolean functions describing the half Subtractor are:  $S = A \oplus B$   $C = A' \cdot B$  Full Subtractor: Subtracting two single-bit binary values, B, Cin from a single-bit value A produces a difference bit D and a borrow out Br bit. This is called full subtraction. The Boolean functions describing the full-subtractor are:  $D = (x \oplus y) \oplus Cin$   $Br = A'B + A'(Cin) + B(Cin)$ .

### I. TO REALIZE HALF ADDER

TRUTH TABLE


INPUTS		OUTPUTS	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

BOOLEAN EXPRESSIONS:



$$S = A \oplus B$$

$$C = A \cdot B$$


i) Basic Gates

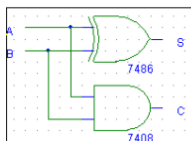

ii) NAND Gates

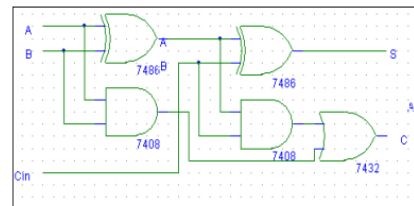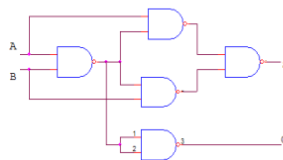

ii) NAND GATES

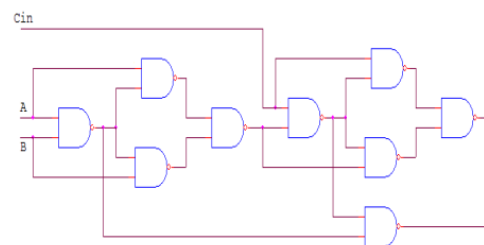

### II. FULL ADDER

TRUTH TABLE

INPUTS			OUTPUTS	
A	B	Cin	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

BOOLEAN EXPRESSIONS:

$$S = A \oplus B \oplus Cin$$

$$C = A \cdot B + B \cdot Cin + A \cdot Cin$$

### III. HALF SUBTRACTOR

TRUTH TABLE


INPUTS		OUTPUTS	
A	B	D	Br
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

BOOLEAN EXPRESSIONS:


$$D = A \oplus B$$

$$Br = \bar{A} \cdot B$$

i) BASIC GATES

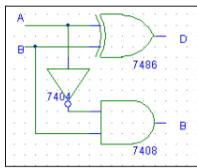

ii) NAND Gates

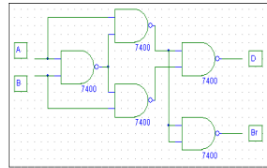

IV. FULL SUBTRACTOR

TRUTH TABLE


INPUTS			OUTPUTS	
A	B	Cin	D	Br
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

BOOLEAN EXPRESSIONS:


$$D = A \oplus B \oplus C$$

$$Br = \bar{A} B + B Cin + \bar{A} Cin$$

i) BASIC GATES

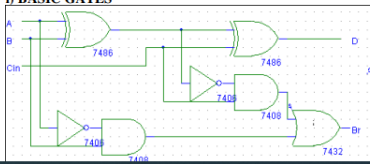

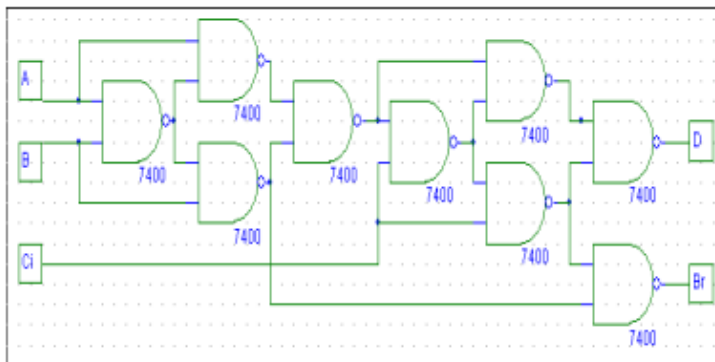ii) To Realize the Full subtractor using NAND Gates only



PROCEDURE:

- Check the components for their working.
- Insert the appropriate IC into the IC base.
- Make connections as shown in the circuit diagram.
- Verify the Truth Table and observe the outputs.

RESULT: The truth table of the above circuits is verified.