

Experiment-3

Aim: Objective of synthesis of flip-flops:


1. to understand the basic concepts of flip-flops as elementary units of sequential circuits
2. to understand what is race around condition and why does it occur in JK flip-flop
3. to know how the race around condition which occurs in JK flip-flop is avoided
4. to understand what kind of problems may occur in master slave JK flip-flop
5. to know the need for master slave JK flip-flop with asynchronous preset and clear

Theory

Synthesis of Flip Flops

Till now the experiments are based only on the combinational circuits where output at any instance depends only on the current input. Most of components of digital logic consists combinational circuits but they likely to have memory elements too. Those type of circuits are known to be *sequential circuits*. In a sequential circuit the present output is not only determined by the present input but also depends on the past output. flip-flops are the simplest kind of sequential circuits. A flip-flop can maintain a binary state identity which means it can act as 1-bit memory cell. There are different kind of flip-flops depending on the number of inputs or the way the inputs affect the states.

Basic flip-flop : A basic flip-flop circuit can be constructed using two cross-coupled NAND/NOR gates shown below . Each flip-flop has two outputs, Q and Q' , and two inputs, *set* and *reset*. When the *set* input goes to 1 the Q output goes to 1 and the Q' goes to 0 when *reset* goes to 1. But when both *set*, *reset* are 1, both Q , Q' outputs go to 0 for basic flip-flop circuit with NOR gates. In basic flip-flop circuit with NAND gates, when both input go to 0, both outputs go to 0 violating the fact that the outputs of the flip-flop have to be complement of each other.

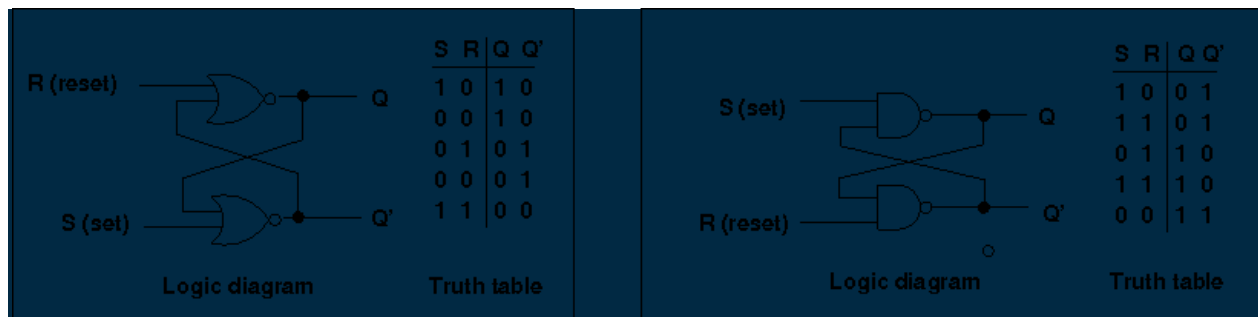


There are various different kind of **flip-flops**. Some of the common flip-flops are: R-S flip-flop, D flip-flop, J-K flip-flop, T flip-flop etc.

1. **Clocked RS flip-flop** : The basic flip-flop is modified by adding some gates to the inputs so that the flip-flop changes state only when the clock pulse is 1. The truth table for this type of flip-flop is shown below. If R is high then reset state occurs and when S=1 then set state. However, if both the inputs are 1 then it violates normal operation of flip-flop.


Q	S	R	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	indeterminate
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	indeterminate

2. **JK flip-flop** JK flip-flop is a refinement of RS flip-flop where the indeterminate state of RS type is defined. Input *J* and *K* are respectively the *set* and *reset* inputs of the flip-flop. When both the inputs are high then the output of the flip-flop switches to its complemented state. A clocked JK flip-flop is shown below.


Q	J	K	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 

 
3. In level triggered JK flip-flops, at $J=1$ and $K=1$, a timing problem, known as race around condition arises which can be explained by the following diagram. Let the width of a clock pulse is t_p and the current output Q is 1. when the clock is applied, after the propagation delay, say dt , the output will toggle and now the output Q will be 0. If dt is less than t_p , then after dt the output Q will again toggle and become 1. Thus the output will oscillate between 0 and 1 within the t_p interval, so at the end of the clock pulse t_p , the output will be ambiguous.



 
4. 0 T
5. Master slave JK flip-flop overcome this race around condition. The following figure depicts the circuit diagram.



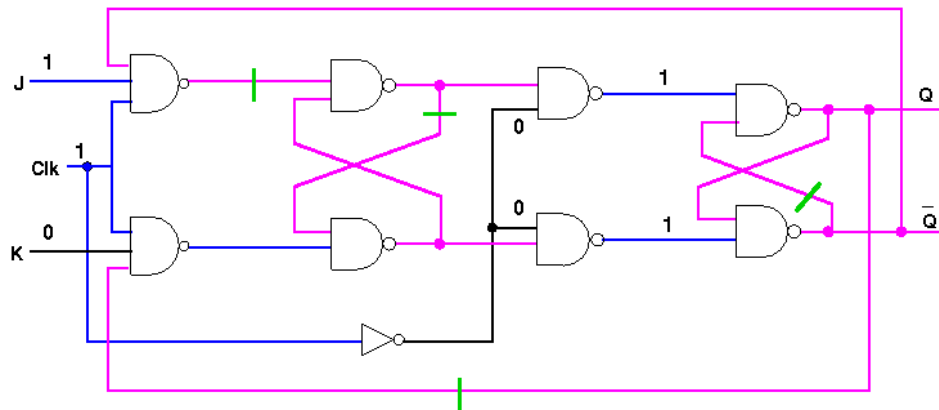7. However, the master slave circuit, though handles race around condition, it may work improperly initially, if it has inconsistent initialization. Ideally, initially the master and the slave should have the same value, but if it does not, then it leads to inconsistent initialization, for which the circuit behaves improperly. Bellow is a case showing the improper output for an inconsistent initialization. Here, at clock=1, the master is supposed to change its state accordingly, but.....




8.

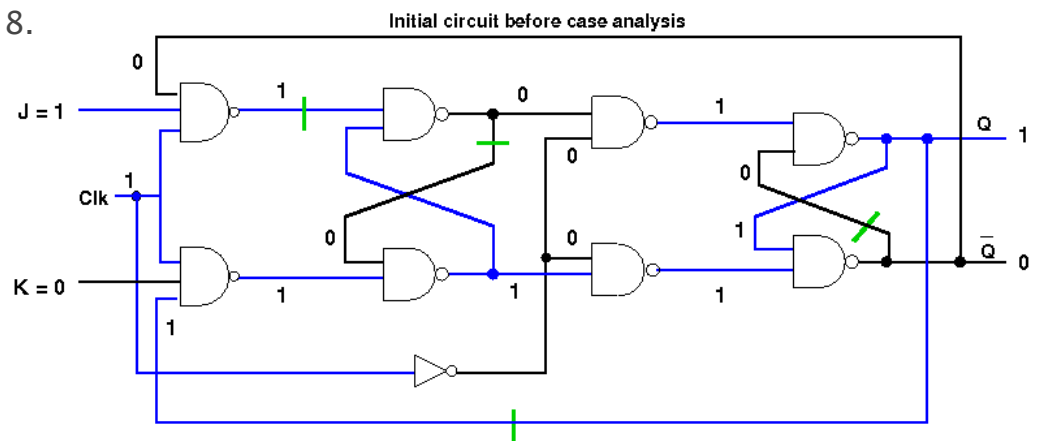

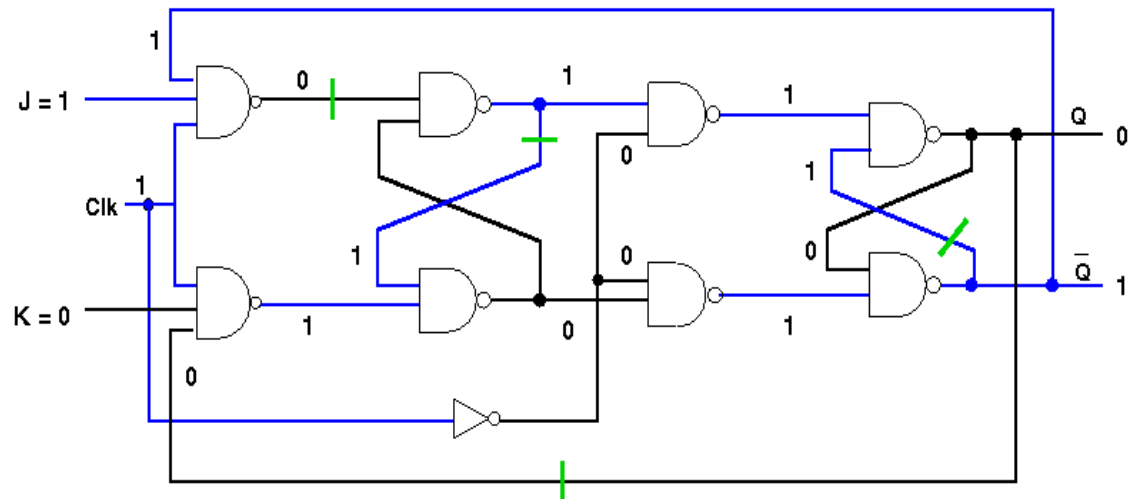9.

Circuit after doing case analysis with setting the unknown back edge values of loops to 0
This shows the inconsistent initialization where master changes its state improperly at clock=1




Circuit after doing case analysis with setting the unknown back edge values of loops to 1

This shows the proper initialization where master changes its state properly at clock=1

10.

 11. The problem occurred due to the inconsistent initialization in the master slave JK flip-flop can be avoided by asynchronously presetting or clearing the flip-flop. The circuit diagram is shown below.




Master slave JK flip-flop with asynchronous preset and clear

12.

13. **D flip-flop** The D flip-flop is used to transfer data to the flip-flop. It is basically the JK flip-flop where the the K input is inverted. The circuit diagram of the D flip-flop is shown below,

Q	D	Q(t + 1)
0	0	0
0	1	1
1	0	0
1	1	1

 

14. **Tflip-flop** The T or "toggle" flip-flop changes its output on each clock edge. The truth table as follows:

Q	T	Q(t + 1)
0	0	0
0	1	1
1	0	1
1	1	0

Procedure

Synthesis of flip-flops:

Guideline to perform the experiment: Synthesis of flip-flops

1. Start the simulator as directed. This simulator supports 5-valued logic.
2. The experiment is needed to be performed on the given structural working modules of all kinds of flip-flops.
3. The flip-flop components are in the sequential circuit drawer in the pallet. The pin configuration is shown whenever the mouse is hovered on any canned component of the palette or press the 'show pinconfig' button. Pin numbering starts from 1 and from the bottom left corner (indicated with the circle) and increases anticlockwise.
4. Click on the flip-flop component in the pallet and then click on the position of the editor window where you want to add the component (no drag and drop, simple click will serve the purpose), likewise add free running clock, bit switches and bit displays (from

Display and Input drawer of the pallet, if it is not seen scroll down in the drawer)

5. To connect any two components select the Connection menu of palette, and then click on the source terminal and click on the target terminal. connect all the components, connect the clock to the clock port of the flip-flop, connect bit switches to the proper input ports of the flip-flop, connect bit displays to the proper output ports of the flip-flop.
6. To see the circuit working, click on the selection tool in the pallet then give input by double clicking on the bit switch, turn on the *case analysis* feature in the simulator if the pin configuration of that flip-flop mentions the case analysis as required, then start the clock now check behavior of the flip-flop according the guideline given in the objective.

Conclusion: Synthesis of flip flop is understood.